

Introduction to Electrical circuits


by Trish Loeblein

phet.colorado.edu

Learning Goals: Students will be able to


- 1. Discuss basic electricity relationships**
- 2. Analyze the differences between real circuits and the simulated ones**
- 3. Build circuits from schematic drawings**
- 4. Use a multimeter to take readings in circuits.**
- 5. Provide reasoning to explain the measurements and relationships in circuits.**

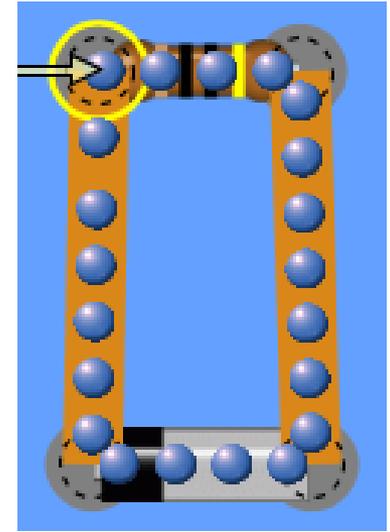1.If you build this circuit with real equipment, how would you determine the resistance of the resistor?




- A. Use the ohmmeter after connecting the battery.
- B. Use the ohmmeter before connecting the battery.
- C. Measure the current and voltage, then use Ohm's law
- D. Two of the above.

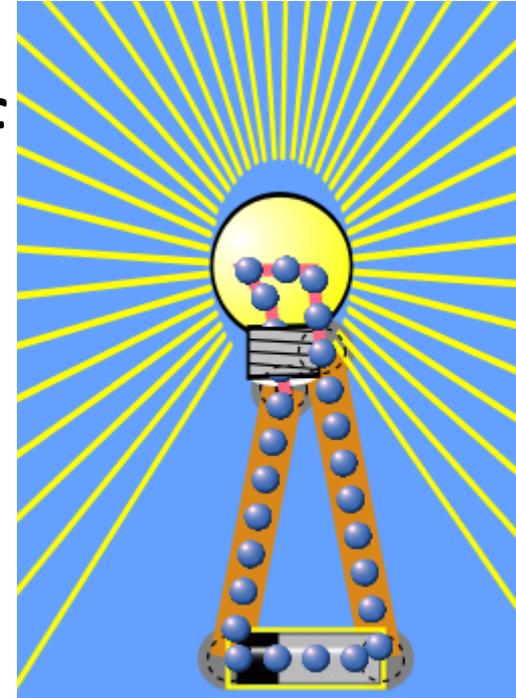2.If you increase the voltage of the battery, how will the light bulb change?




- A. It will be look brighter because the yellow lines are brighter and longer
- B. It will be less bright because the yellow lines are less bright and shorter
- C. There is no change because the bulb just uses the extra energy without changing brightness

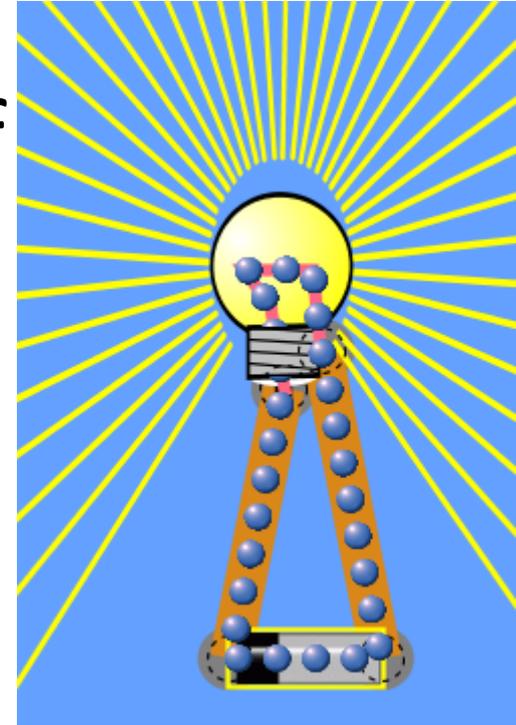3. If you increase the voltage of the battery, how will the electron display  change?




- A. The blue dots will get bigger to show more energy is being used**
- B. The blue dots will move faster to show more energy is being used**
- C. There is no change**

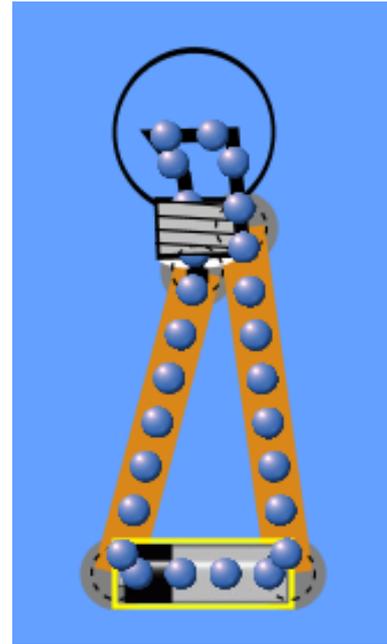4. If you build circuit A and then add a resistor as in circuit B, the light will



A

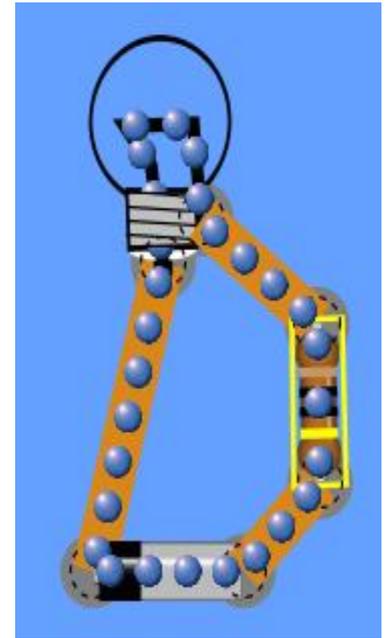

B

- A. Look brighter**
- B. Look less bright**
- C. There will no change in brightness**