

Parallel Circuits

Name: _____

	Battery Voltage	Current		Voltage Drop	Calculated Resistance (V drop/ Br.Current)	Total Resistance (Batt. V/ OverallCurrent)
		Overall	Branch Current			
	(V)	(A)	(A)	(V)	(Ω)	(Ω)

Single Branch Parallel Circuit						
--------------------------------	--	--	--	--	--	--

Two Branch Parallel Circuit			#1		
			#2		

Three Branch Parallel Circuit			#1		
			#2		
			#3		

Right click on the resistors to change the resistance to the values below.

Total Resistance

Complex 20 & 30 Ω			#1	10	
			#2	10	
			#3	20	
				30	

Short Circuit			#1	10	
			#2	10	
			#3	20	
				30	
			Short	0	

What is the relationship between the battery voltage and the voltage drops?

How do the currents compare in a parallel circuit?

- A) What happens to the overall current as more branches are added to the circuit?
- B) How does the branch current compare as resistors are added within the branch?

What is the relationship to the total resistance and the individual resistors?