

Ohm's Law

Grade: 9th - 10th

Brief Concepts:

- **Ohm's law:** Current flowing through a resistor is directly proportional to the potential applied across it.

$$V = I \times R$$

- **Series connection:** Cells are joined end to end in a series connection. Positive terminal of a cell is connected to negative terminal of the next cell.

Explore:


1. Select a value of resistance. Now, increase the potential across resistor. How does current change?
2. Select a value of potential. Now, increase resistance. How does the current change?
3. If a battery of 9 volt is connected across resistor of 1000 ohm, what will be the value of current flowing through it?
4. For a resistor of 10 ohm, apply five different potentials and measure current through resistor. Plot Potential (V) v/s Current (I) curve on graph paper.

| Potential (Volt) | 1.5 Volt | 3 Volt | 4.5 Volt | 6 Volt | 7.5 Volt |
|------------------|----------|--------|----------|--------|----------|
| Current (Amp) | | | | | |

5. Measure slope of this curve. How does this slope relate with resistance? If the value of resistance were 50 Ohm instead of 10 Ohm, how will this slope change?

Think:

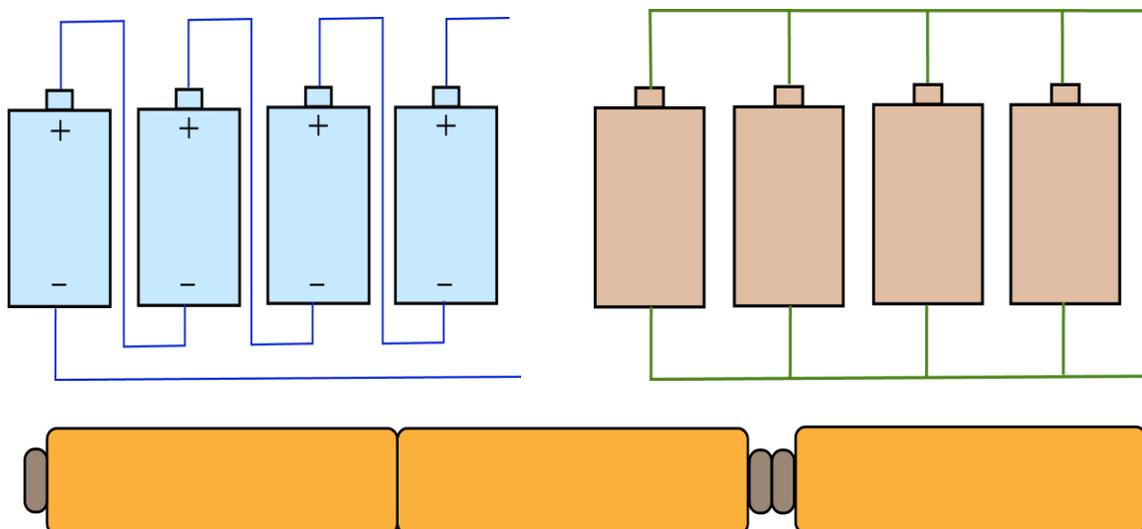1. Which among the following connections is a series connection?



2. If you need to make 9 Volt battery by using 1.5 Volt cells, how many minimum cells you will need? And how will you connect them?

Contributions:

Author: SK Gupta (MS, Indian Institute of Technology Madras)

Editor: Chaithra Navada (Integrated MA, Indian Institute of Technology Madras)

Illustration: Sanjana Acharya (Integrated MA, Indian Institute of Technology Madras)

Contact Information: For any corrections/suggestions, please mail us at athenescience@gmail.com

Website: www.athenescience.org (This write-up can be accessed on our website for free)