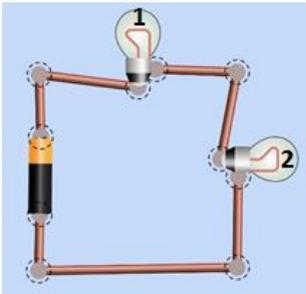


## Activity: Measuring Current and Voltage


### Part 1: Prediction Questions - comparing circuits

Consider the pictures of each of these circuits, then answer the questions below. Answer the prediction questions before you build these circuits:


**Series Circuit**



**Parallel Circuit**

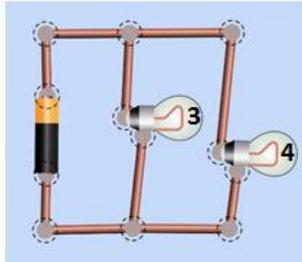

**Complex Circuit**



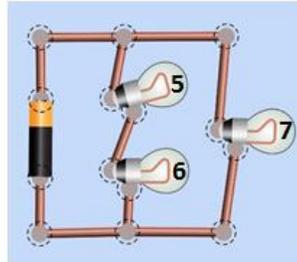


1) From the circuits above, predict which bulb (or bulbs) will be the brightest. Why do you think that?

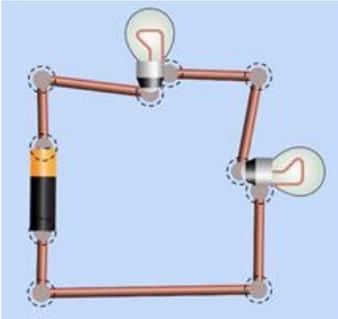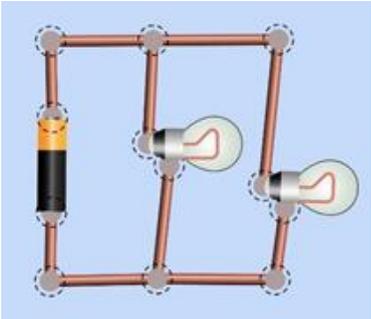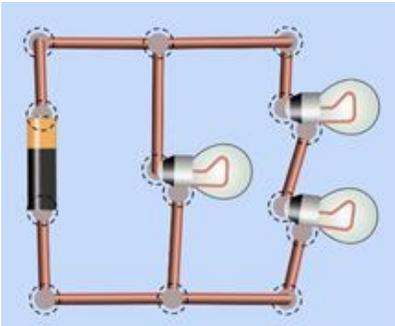2) Current is the flow of charge (measured in coulombs/sec = amps) in a circuit. Describe how you think current will flow in the different types of circuits above.






<p>2) Series Circuit</p> 	<hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/>	<hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/>	
<p>3) Parallel Circuit</p> 	<hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/>	<hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/>	
<p>4) Complex circuit</p> 	<hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/>	<hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/> <hr/>	

**Summary (your rule):**

1. Compare the patterns you see in a series circuit to the ones you see in parallel and complex circuits. Try to establish the rules about voltage and current for each type of circuit.  
For example, "In a series circuit, I see that the current ....., whereas in a parallel circuit I see...".

### Analysis Questions

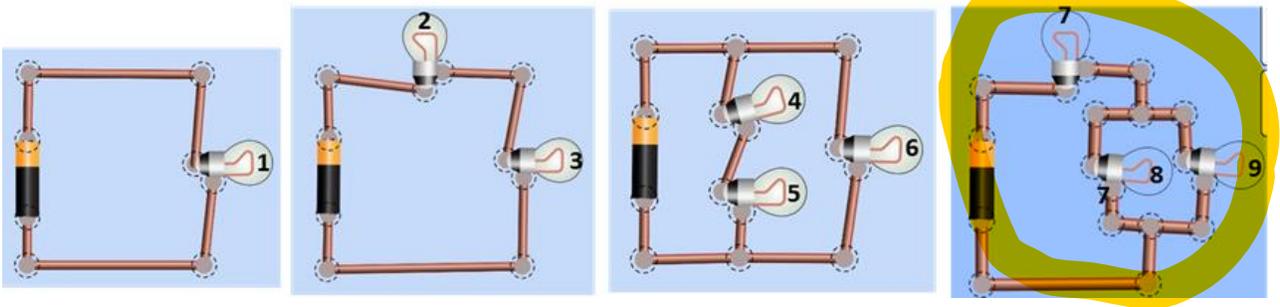- 1) From your rules above, sort (or list) the light bulbs in these circuits from brightest to dimmest (i.e greatest current to least current). Some bulbs might be the same brightness.



a) (sort the bulbs by brightness)

b) After you make your rankings, build some circuits to check your answers and list the correct ranking below.

c) Did your rules allow you to correctly rank the bulb brightness?

d) If yes, explain the ranking using your rules.

If no, describe changes you can make to improve your rules.

- 2) You have two batteries and a lightbulb, and you want to make a flashlight. Draw how you would hook them up to make the brightest flashlight, and explain why.

